



UNITED STATES
AIR FORCE
ACADEMY





UNITED STATES
AIR FORCE
ACADEMY

ECE 281 Lesson 10



Lesson 10 Outline

- Do Time Logs!
- Lab 1 In-class

Breadboards 101

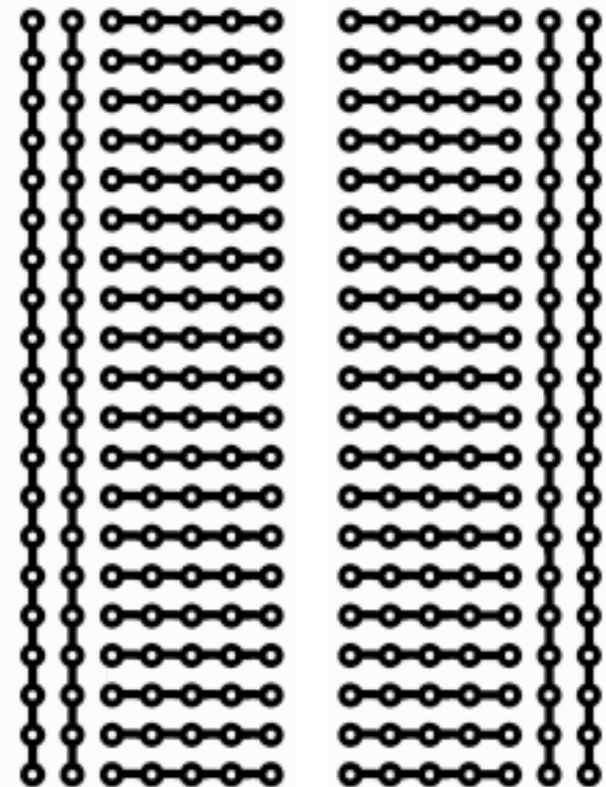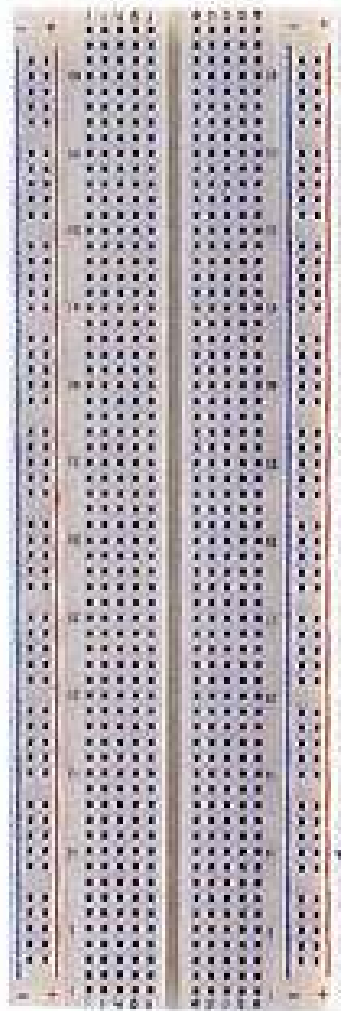


8:1 Multiplexer (PN 74151)

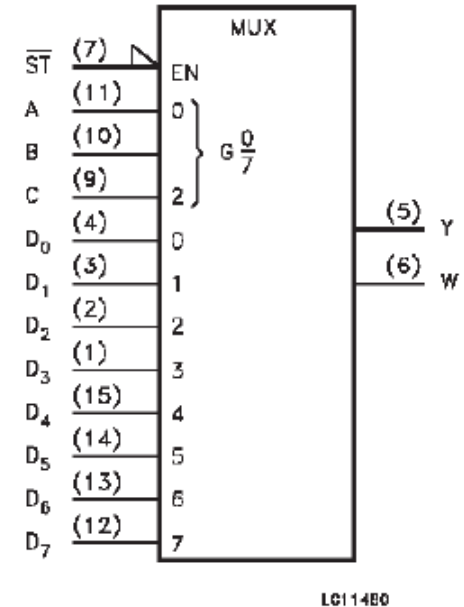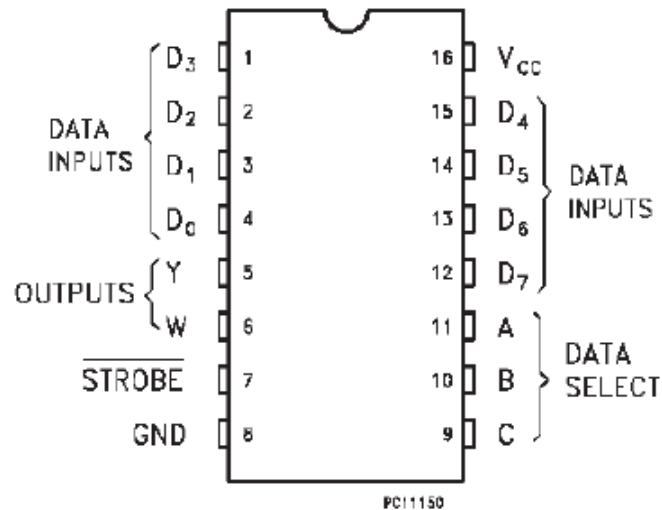

■ <K:\DF\DFEC\ECE281\Datasheets\74x151.pdf>

8:1 Multiplexer (PN 74151)

INPUT AND OUTPUT EQUIVALENT CIRCUIT

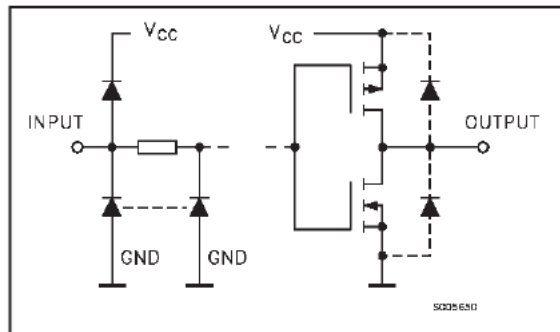

PIN DESCRIPTION

PIN No	SYMBOL	NAME AND FUNCTION
4, 3, 2, 1, 15, 14, 13, 12	D ₀ to D ₇	Multiplexer Inputs
5	Y	Multiplexer Output
6	W	Complementary Multiplexer Output
7	STROBE	Strobe Input
11, 10, 9	A, B, C	Select Inputs
8	GND	Ground (0V)
16	V _{CC}	Positive Supply Voltage

TRUTH TABLE

INPUTS				OUTPUTS	
SELECT			STROBE	Y	W
C	B	A	S		
X	X	X	H	L	H
L	L	L	L	D ₀	<u>D₀</u>
L	L	H	L	D ₁	<u>D₁</u>
L	H	L	L	D ₂	<u>D₂</u>
L	H	H	L	D ₃	<u>D₃</u>
H	L	L	L	D ₄	<u>D₄</u>
H	L	H	L	D ₅	<u>D₅</u>
H	H	L	L	D ₆	<u>D₆</u>
H	H	H	L	D ₇	<u>D₇</u>

X : Don't Care

■ <K:\DF\DFEC\ECE281\Datasheets\74x151.pdf>

Hex NOT (PN 7404)


SN5404 . . . J PACKAGE

SN54LS04, SN54S04 . . . J OR W PACKAGE

SN7404, SN74S04 . . . D, N, OR NS PACKAGE

SN74LS04 . . . D, DB, N, OR NS PACKAGE


(TOP VIEW)

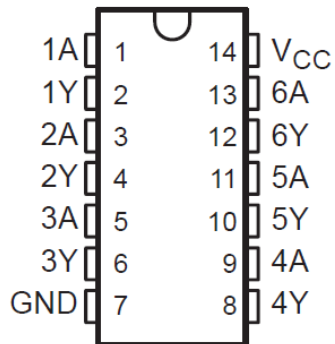

FUNCTION TABLE
(each inverter)

INPUT A	OUTPUT Y
H	L
L	H

logic diagram (positive logic)

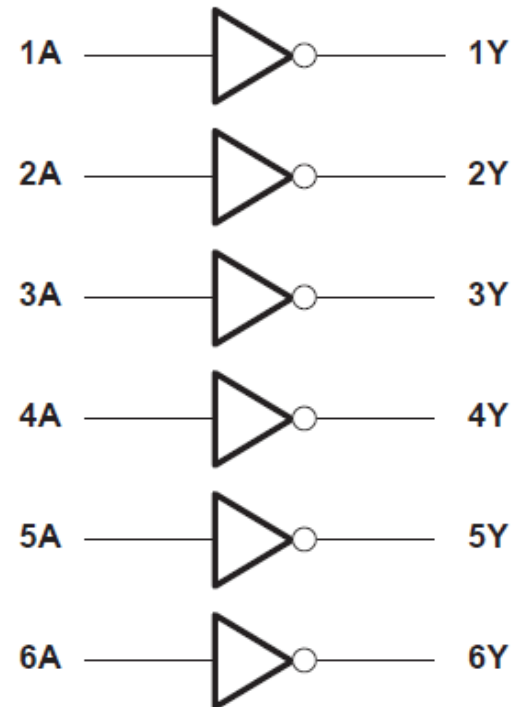

$$Y = \overline{A}$$

■ <K:\DF\DFEC\ECE281\Datasheets\sn74ls04.pdf>

-
- Test as you go
 - Connect ground and power first
 - Test one chip at a time
 - Then connect chips together

 - Keep wires as flat and straight as possible
 - Do not cross wires if you can avoid it



UNITED STATES
AIR FORCE
ACADEMY



UNITED STATES
AIR FORCE ACADEMY